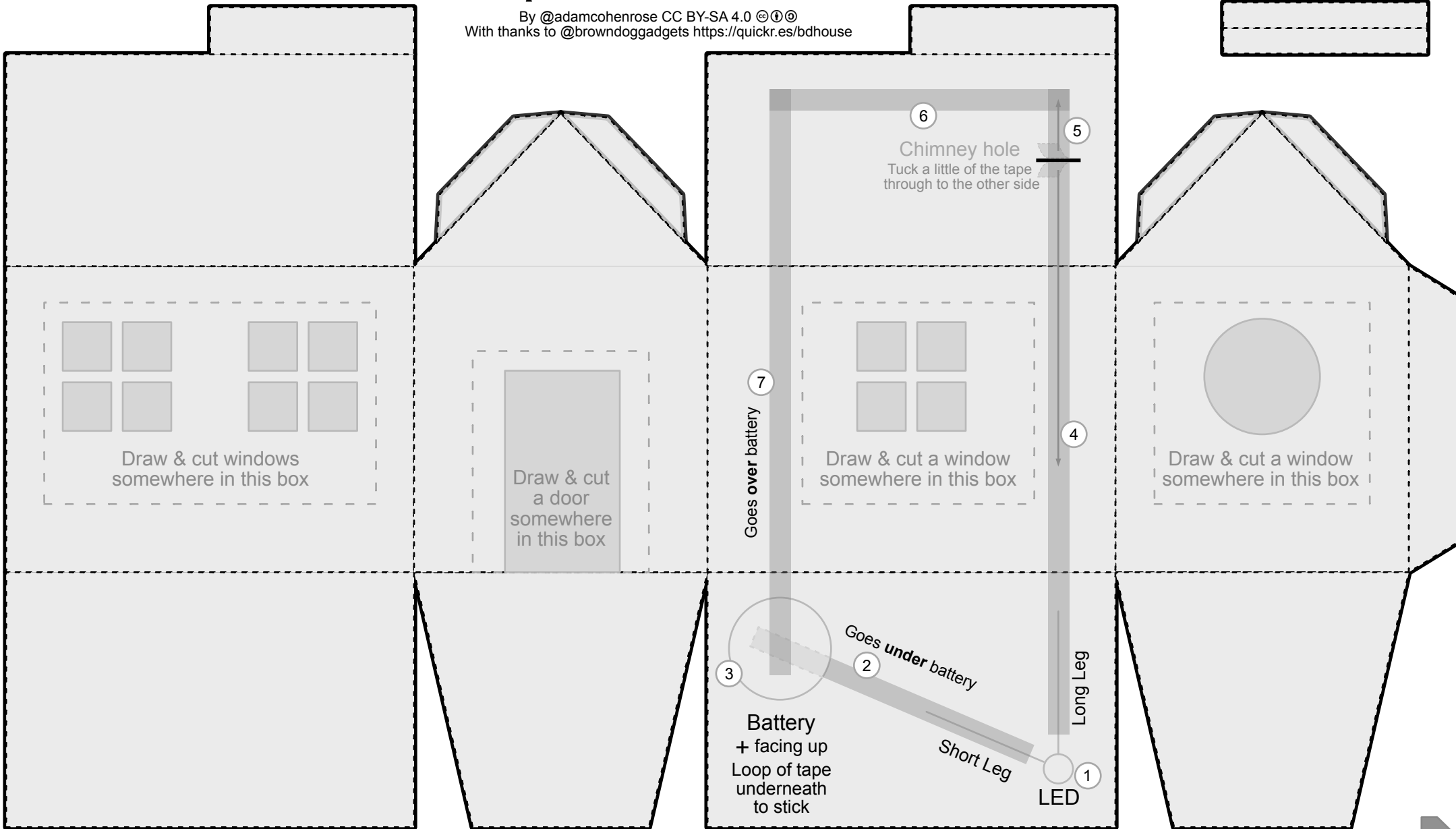


Paper circuit house

By @adamcohenrose CC BY-SA 4.0 © ① ②
 With thanks to @browndoggadgets <https://quicker.es/bdhouse>

Don't forget the chimney!



- Draw your windows & doors
- Ask an adult to help cut them out
- Cut along solid outlines
- Colour in the back
- Fold along dotted lines

- Follow the numbers to build your circuit
- Stick tape 2 **under** the battery
- Stick the battery to tape 2 with a loop of tape
- Tape 4 and 5 should poke through the chimney hole and stick to the other side of the paper

- Stick tape 7 **over** the battery
- Fold the chimney in half lengthways
Then stick a piece of tape around it lengthways
You should end up with a tape "lolly" that will be a switch when stuck in the chimney hole

