


Slot A

Slot B

Fold top half of card towards you

Paper circuit light-up card

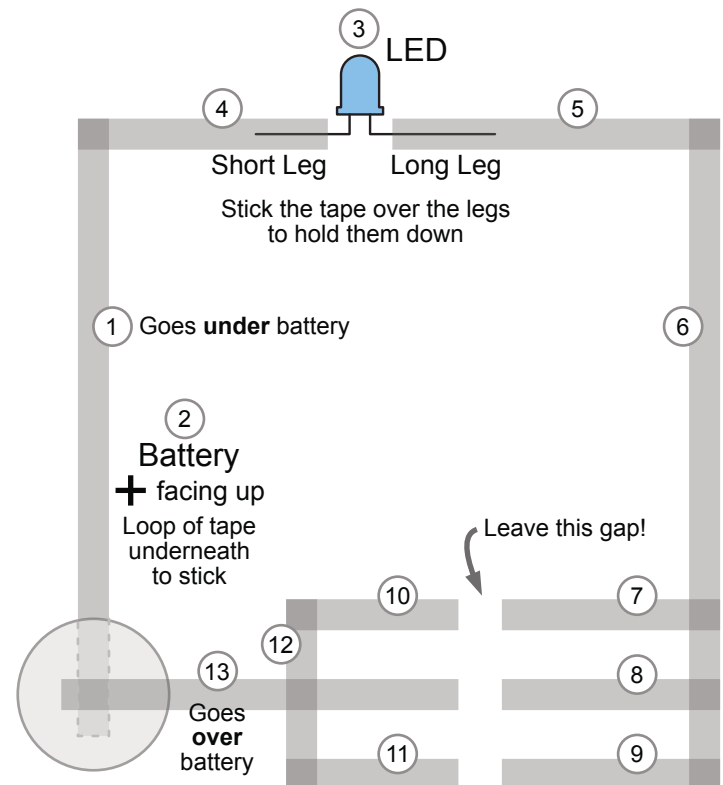By @adamcohenrose CC BY-SA 4.0 © ⓘ ⓘ
Inspired by lainealison
See more at <https://quicker.es/papercircuits>



- Cut the slider off and fold it
- Follow the numbers for the circuit
- Fold the card
- Fit the slider: Tab A → Slot A; Tab B → Slot B with the tape facing down & folded parts on top
- Stick Tab A in place
- Draw inside your light-up card

