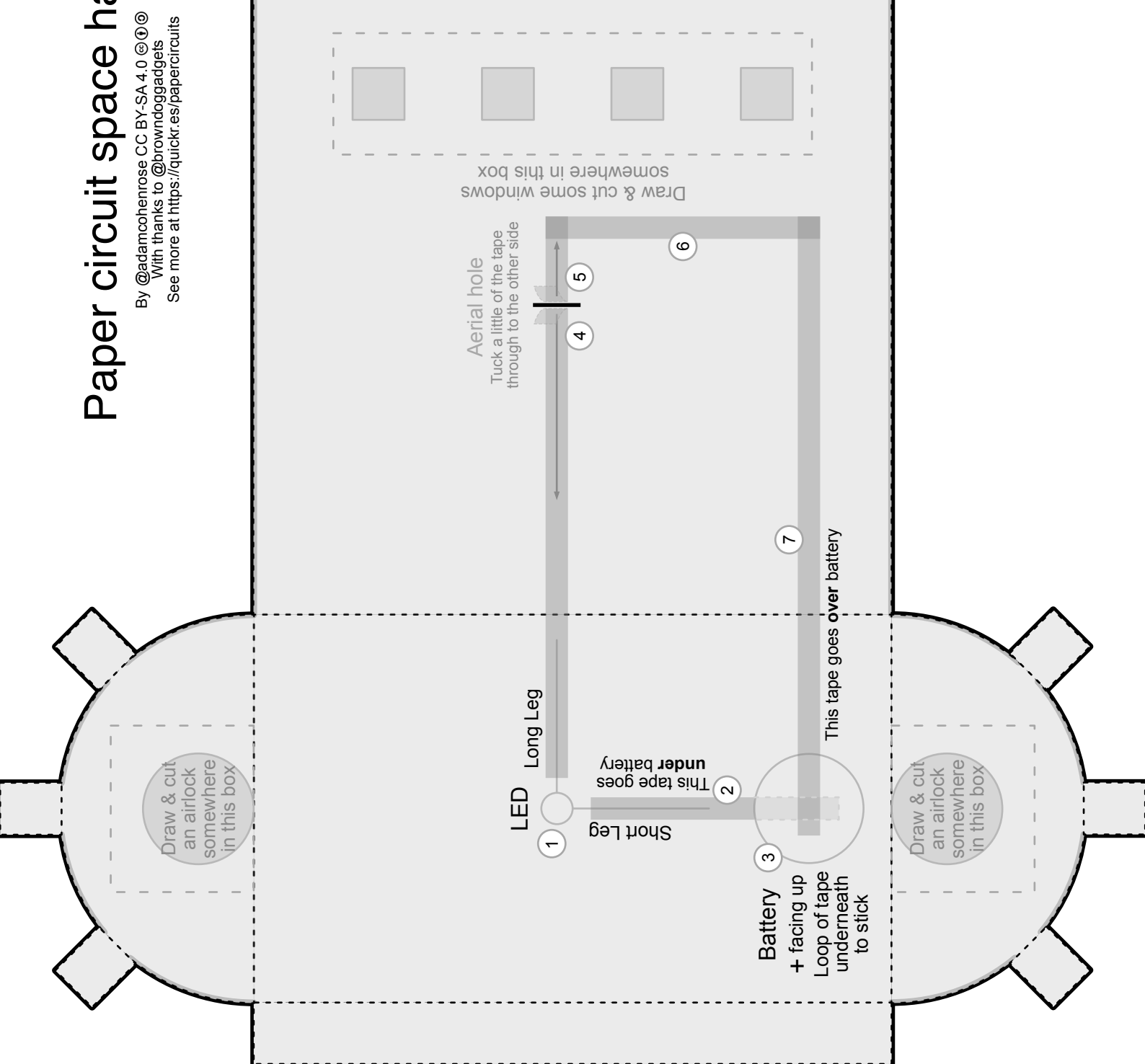


Paper circuit space habitat

By @adamcohenrose CC BY-SA 4.0 ©
With thanks to @browndoggadgets
See more at <https://quickr.es/papercircuits>



Instructions

- Draw your windows & doors
- Ask an adult to help cut them out
- Cut along solid outlines
- Colour in the back
- Fold along dotted lines
- Follow the numbers to build your circuit
- Stick tape 2 **under** the battery
- Stick the battery to tape 2 with a loop of tape
- Tape 4 and 5 should poke through the aerial hole and stick to the other side of the paper
- Stick tape 7 **over** the battery
- Fold the aerial in half lengthways
- Then stick a piece of tape around it lengthways as shown to the right => You should end up with a tape "lolly" that will be a switch when poked through the aerial hole



Don't forget to cut out the aerial!!

